

Lecture 30, Mar 28, 2022

KVL and KCL in the Phasor Domain

- Regular KVL on a loop gives

$$\sum_{i=1}^n v_i(t) = 0$$

$$\implies \sum_{i=1}^n V_i \cos(\omega t + \alpha_i) = 0$$


$$\implies \operatorname{Re} \left\{ \sum_{i=1}^n V_i e^{j\alpha_i} e^{j\omega t} \right\} = 0$$

$$\implies \operatorname{Re} \left\{ \left(\sum_{i=1}^n V_i e^{j\alpha_i} \right) e^{j\omega t} \right\} = 0$$

$$\implies \sum_{i=1}^n \mathbf{V}_i = 0$$
- Similarly for KCL on a node, $\sum_{i=1}^n \mathbf{I}_n = 0$
- Both KVL and KCL hold in the phasor/frequency domain

Impedance


- Consider a general circuit element:

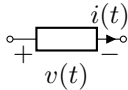


- Suppose $v(t) = V_m \cos(\omega t + \theta_v)$ and $i(t) = I_m \cos(\omega t + \theta_i)$
- *Impedance* for this element is defined as $\mathbf{Z} = \frac{\mathbf{V}}{\mathbf{I}} = \frac{V_m \angle \theta_v}{I_m \angle \theta_i} = \left(\frac{V_m}{I_m} \right) \angle (\theta_v - \theta_i)$ where \mathbf{V} and \mathbf{I} are the phasors for the voltage and current (assuming PSC)
 - Impedance is similar to resistance in a DC circuit
 - Unit for impedance is ohms
 - Expressed in rectangular form, $\mathbf{Z} = R + jX$
 - * The real part R is the *resistance*
 - * The imaginary part X is the *reactance*
 - * Both have units of ohms
- Similar to conductance in DC circuits, for AC define the *admittance* as $\mathbf{Y} = \frac{\mathbf{I}}{\mathbf{V}} = \frac{1}{\mathbf{Z}}$
 - Admittance has the same units as conductance, Siemens or mhos
 - Expressed in rectangular form, $\mathbf{Y} = G + jB$, where G is the *conductance*, and B is the *susceptance*, both having units of Siemens

Impedance Relations for Passive Components

- For a resistor:

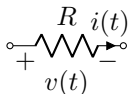

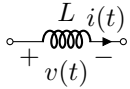
- $\mathbf{Z}_R = \frac{\mathbf{V}}{\mathbf{I}} = \frac{RI}{\mathbf{I}} = R$
 - * The impedance of a resistor is just the resistance of that resistor
 - * A resistor has no reactance; voltage and current are always in phase
- For an inductor:



$$- \mathbf{Z}_L = \frac{\mathbf{V}}{\mathbf{I}} = \frac{j\omega L \mathbf{I}}{\mathbf{I}} = j\omega L$$

- * The impedance of an inductor is entirely imaginary, i.e. it has no resistance but ωL reactance
- * Note the impedance is dependent on frequency; when $\omega \rightarrow 0$, $\mathbf{Z}_L \rightarrow 0$, and when $\omega \rightarrow \infty$, $\mathbf{Z}_L \rightarrow \infty$
- * An inductor affects higher frequency signals more
- * Intuitively, decreasing the frequency makes the current closer to DC conditions, under which the inductor is a short circuit

- For a capacitor:

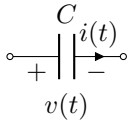

$$- \mathbf{Z}_C = \frac{\mathbf{V}}{\mathbf{I}} = \frac{\mathbf{V}}{j\omega C \mathbf{V}} = \frac{1}{j\omega C} = -\frac{j}{\omega C}$$

- * The impedance of a capacitor is also pure imaginary; resistance is zero and reactance is $-\frac{1}{\omega C}$
- * When $\omega \rightarrow 0$, $\mathbf{Z}_C \rightarrow \infty$; when $\omega \rightarrow \infty$, $\mathbf{Z}_C \rightarrow 0$
- * A capacitor affects lower signal frequencies more
- * Intuitively, lower frequencies are closer to DC conditions, under which a capacitor is an open circuit

Equivalent Impedances

- Consider a number of impedance elements in series; all elements have the same \mathbf{I} so across each there is a voltage of $\mathbf{V}_i = \mathbf{Z}_i \mathbf{I}$, so $\mathbf{V} = \mathbf{I} \sum_{i=1}^n \mathbf{Z}_i \implies \frac{\mathbf{V}}{\mathbf{I}} = \sum_{i=1}^n \mathbf{Z}_i$
- The equivalent impedance for a series connection is $\mathbf{Z}_{eq} = \sum_{i=1}^n \mathbf{Z}_i$
- For a parallel connection the impedance is $\frac{1}{\mathbf{Z}_{eq}} = \sum_{i=1}^n \frac{1}{\mathbf{Z}_i}$